
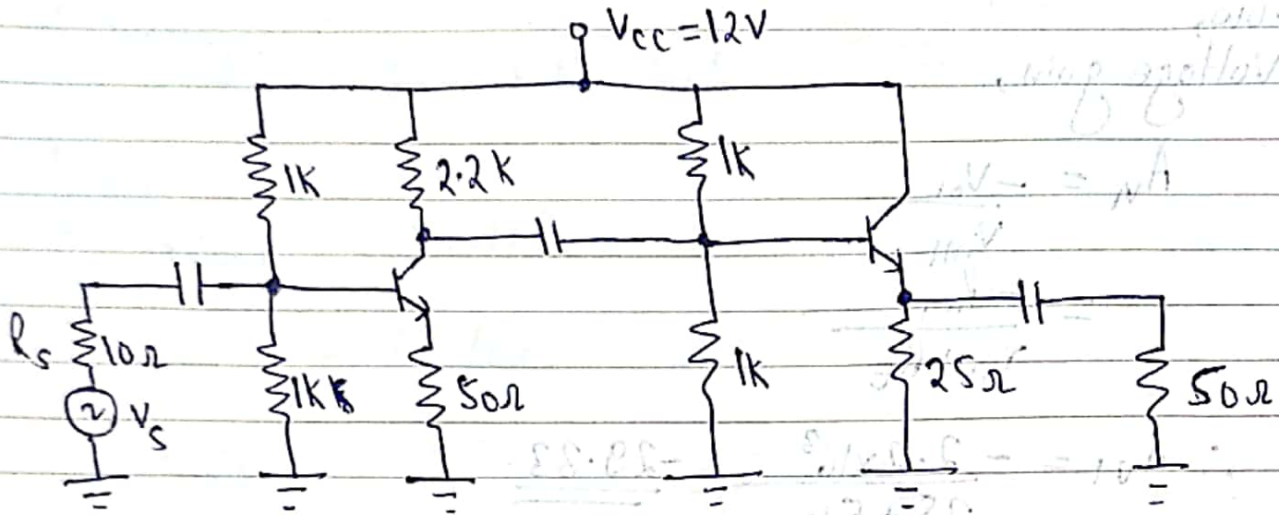


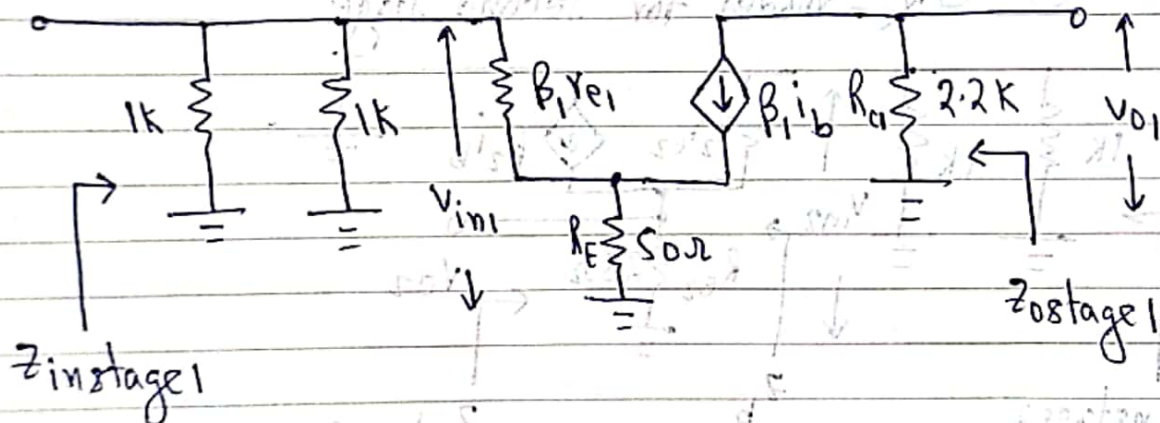- 1) Find overall voltage gain (V_L/V_S) and overall current gain (i_L/i_S) in dB for the cascaded BJT amplifier shown below. (Assume $r_{e1} = r_{e2} = 25\Omega$ & $\beta_1 = \beta_2 = 100$)



Solⁿ Here,
re-model for first stage,



Now,

$$\begin{aligned} Z_{instage1} &= 1K // 1K // \beta_1 (r_{e1} + R_E) \\ &= 1K // 1K // 100 \left(\frac{25}{1000} + \frac{50}{1000} \right) \\ &= 1K // 1K // 7.5K \end{aligned}$$

$$\therefore Z_{instage1} = \frac{1 \times 1 \times 7.5}{1 \times 1 + 1 \times 7.5 + 1 \times 7.5} = \underline{\underline{0.468K}}$$

Again,


$$Z_{\text{ostage1}} = \underline{2.2K} \Rightarrow R_{c1}$$

Now,
 voltage gain,

$$A_{v1} = \frac{-V_{o1}}{V_{in1}} = \frac{-R_{c1}}{r_{e1} + R_E}$$

$$\therefore A_{v1} = \frac{-2.2 \times 10^3}{25 + 50} = \underline{\underline{-29.33}}$$

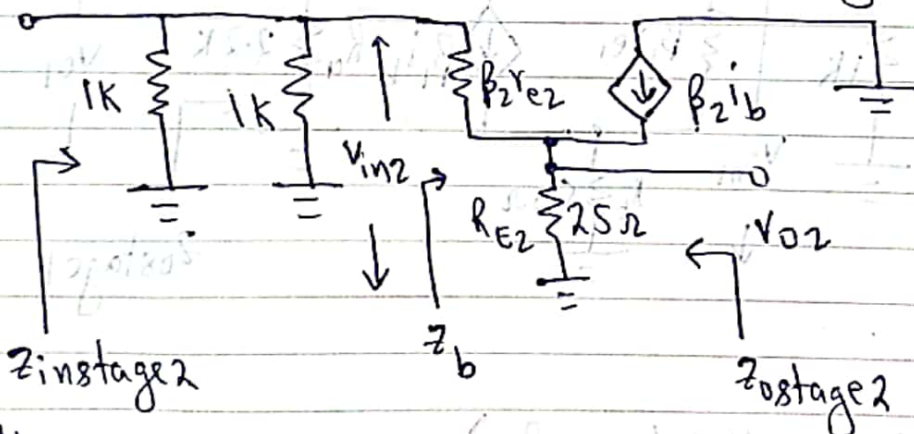voltage gain,
 r_e -model for second stage



Now,

$$Z_{\text{instage2}} = 1K // 1K // Z_b$$

where,

$$Z_b = \beta_2 (r_{e2} + R_{E2})$$

$$= 100 \left(\frac{25}{1000} + \frac{25}{1000} \right) = 5K$$

$$\therefore Z_b = 5K$$

Hence,

$$Z_{instage2} = 1K // 1K // 5K$$

$$\therefore Z_{instage2} = \frac{1 \times 1 \times 5}{1 \times 1 + 1 \times 5 + 1 \times 5} = \underline{\underline{0.454K}}$$

Again,

$$Z_{ostage2} = r_{e2} // R_{E2}$$

$$= 25 // 25 = 12.5K\Omega$$


$$\therefore Z_{ostage2} = 12.5K\Omega = \underline{\underline{0.0125K}}$$

Now, voltage gain;

$$A_{V2} = \frac{R_{E2}}{r_{e2} + R_{E2}}$$

$$\therefore A_{V2} = \frac{25}{25 + 25} = \underline{\underline{0.5}}$$

Now,

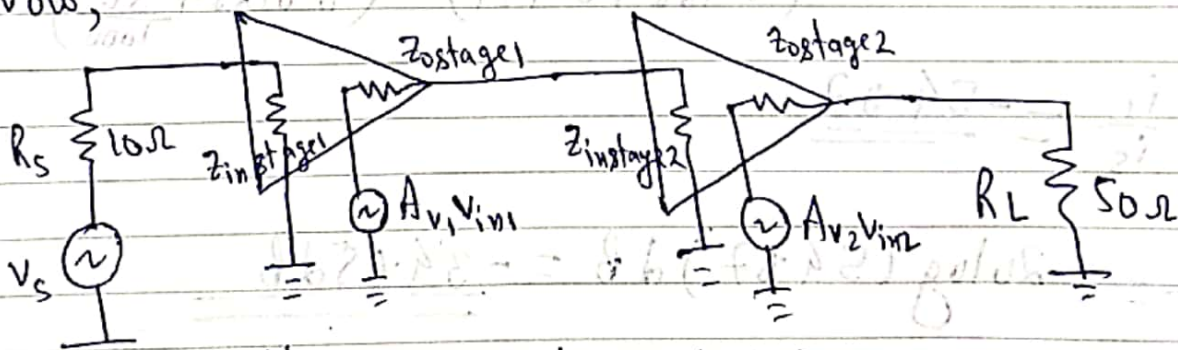Overall voltage gain ($A_{Vs} = V_L / V_s$)

$$V_L / V_s = \left(\frac{Z_{instage1}}{R_s + Z_{instage1}} \right) \times A_{V1} \times \left(\frac{Z_{instage2}}{Z_{ostage1} + Z_{instage2}} \right) \times A_{V2} \times \left(\frac{R_L}{Z_{ostage2} + R_L} \right)$$

$$\text{or, } \frac{V_L}{V_S} = \frac{0.468}{\left(\frac{10}{1000} + 0.468\right)} \times (-29.33) \times \left(\frac{0.454}{2.2 + 0.454}\right) \times (0.5) \times \frac{(50/1000)}{\left(0.0125 + \frac{50}{1000}\right)}$$

$$\therefore \frac{V_L}{V_S} = \underline{\underline{-1.964}}$$

$$\therefore \frac{V_L}{V_S} = -20 \log(1.964) \text{ dB} = \underline{\underline{-5.86 \text{ dB}}} \Rightarrow A_{VS}$$

Again,

Overall current gain ($A_{IS} = i_L / i_S$)

$$\frac{i_L}{i_S} = A_{V1} \times A_{V2} \times \left(\frac{Z_{\text{instage1}}}{Z_{\text{instage1}} + Z_{\text{instage2}}} \right) \times \left(\frac{Z_{\text{instage2}}}{Z_{\text{instage2}} + R_L} \right)$$


$$= -29.33 \times 0.5 \times \left(\frac{0.468}{0.468 + 0.454} \right) \times \left(\frac{0.454}{0.0125 + \frac{50}{1000}} \right)$$

$$\therefore \frac{i_L}{i_S} = \underline{\underline{-54.07}}$$

$$\therefore \frac{i_L}{i_S} = -20 \log(54.07) \text{ dB} = \underline{\underline{-34.65 \text{ dB}}}$$

2) In a balanced network, arm AB consist of a resistance of 500Ω in series with an inductor of $0.18H$, arm BC and arm DA are non-inductive resistances of 1000Ω each and arm CD is unknown. A potential difference of $5V$ at a frequency $5000/2\pi$ is applied between points A & C. Determine the constants of unknown arm.

Solⁿ Here,

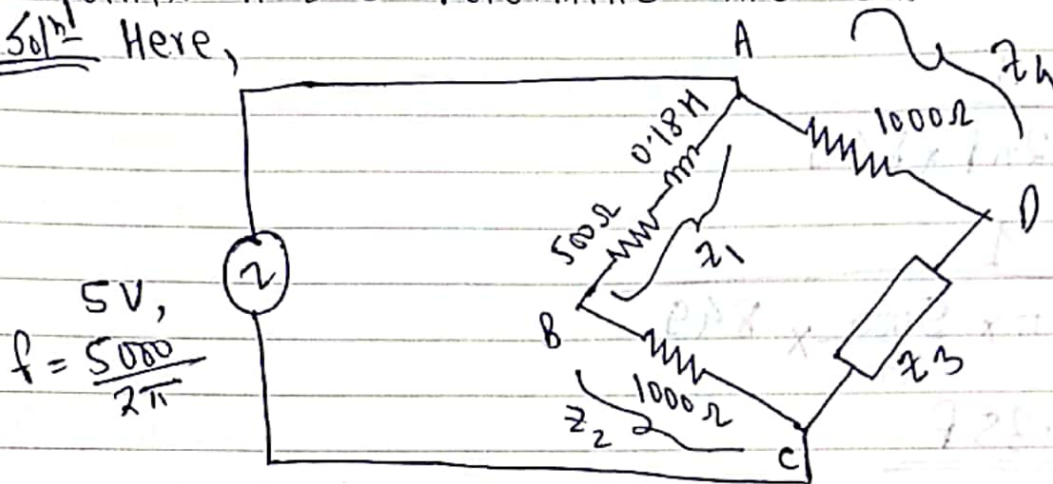

$$\text{Now, } Z_1 = R + j\omega L = 500 + j2\pi f L$$

$$\text{or, } Z_1 = 500 + j2\pi \times \frac{5000}{2\pi} \times 0.18$$

$$\therefore Z_1 = 500 + j900 = \underline{\underline{1029.56 \angle 60.94}}$$

$$Z_2 = 1000\Omega = 1000 \angle 0$$

$$Z_3 = \text{unknown}$$

$$Z_4 = 1000\Omega = 1000 \angle 0$$

we know,

At balance condition,

$$Z_1 Z_3 = Z_2 Z_4$$

$$\therefore Z_3 = \frac{Z_2 Z_4}{Z_1} = \frac{(1000 \angle 0)(1000 \angle 0)}{1029.56 \angle 60.94}$$

$$\therefore Z_3 = 971.28 \angle -60.94 = \underline{\underline{(471.77 - j849)\Omega}}$$

This unknown branch contains resistor & capacitor in series. where,

$$\text{Resistance (R)} = \underline{471.77 \Omega} \quad \left| \begin{array}{l} \text{comparing with,} \\ Z_3 = R - jX_C \end{array} \right.$$

Also,

$$X_C = \frac{1}{2\pi fC} = 849$$

$$\text{or, } C = \frac{1}{2\pi f \times 849}$$

$$\text{or, } C = \frac{1}{2\pi \times \frac{5000}{2\pi} \times 849}$$

$$\therefore C = \underline{2.35 F}$$

Hence,

unknown arm CD contains Resistor (R) = 471.77 Ω in series with capacitor (C) = 2.35 F