

For  $M=3$

$$v/p = V_{ref} \left[ \frac{b_0}{8} + \frac{b_1}{4} + \frac{b_2}{2} \right]$$

For  $n$  bits:

$$V_{p-2p} = V_{ref} \left[ \frac{b_0}{2^n} + \frac{b_1}{2^{n-1}} + \frac{b_2}{2^{n-2}} + \dots + \frac{b_{n-1}}{2^1} \right]$$

Hence,

o/p voltage is:



$$V_o = V_{ref} \left( \frac{-R_f}{R} \right) \left[ \frac{b_0}{2^n} + \frac{b_1}{2^{n-1}} + \frac{b_2}{2^{n-2}} + \dots + \frac{b_{n-1}}{2^1} \right]$$

Also,

$$V_o = -V_{ref} \left( \frac{R_f}{R} \right) \left[ \frac{b_0}{2^n} + \frac{b_1}{2^{n-1}} + \frac{b_2}{2^{n-2}} + \dots + \frac{b_{n-1}}{2^1} \right]$$

Again,

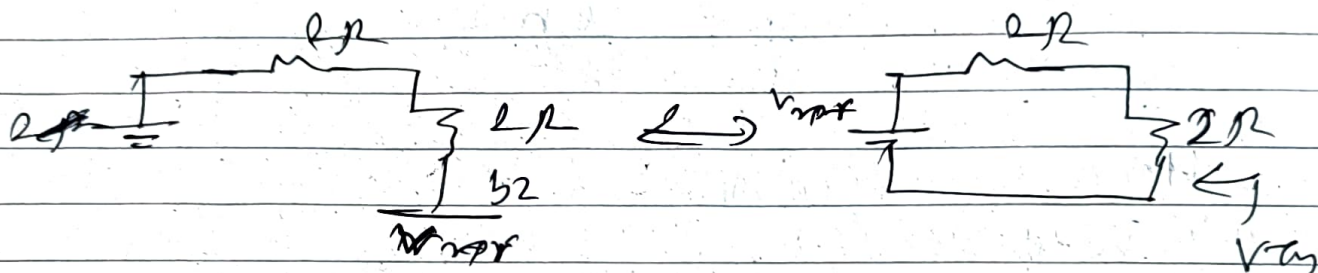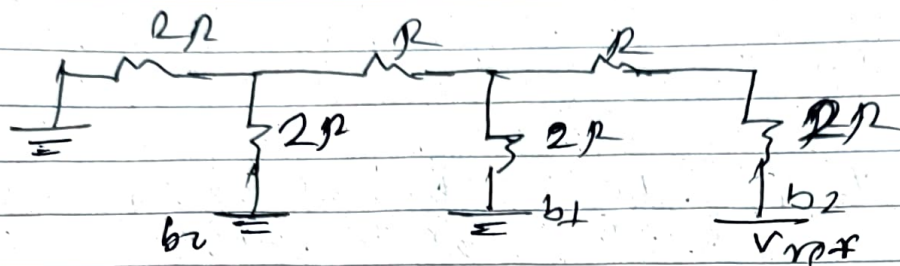$b_2$      $b_1$      $b_0$   
 $\downarrow$      $\downarrow$      $\downarrow$   
 $1$      $0$      $0$



$$V_{th} = \frac{2R}{2R + 2R} \times V_{out} = \frac{V_{out}}{2}$$

Let  $V_{out} = 0$


$$R_{th} = 2R \parallel 2R = R$$

Hence the o/p of ladder network =  $\frac{V_{out}}{2}$

Hence

$b_2$	$b_1$	$b_0$	
1	0	1	$\rightarrow \frac{V_{out}}{8}$
0	1	0	$\rightarrow \frac{V_{out}}{4}$
<del>1</del>	0	0	$\rightarrow \frac{V_{out}}{2}$

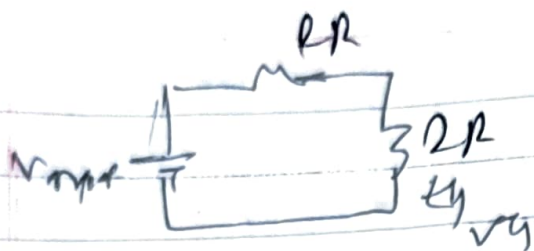
$$1 \cdot 1 \cdot 1 \rightarrow \frac{V_{out}}{2} + \frac{V_{out}}{4} + \frac{V_{out}}{8}$$



$$V_{th} = \frac{2R}{2R + 2R} \times V_{max} = \frac{V_{max}}{2}$$

Let  $V_{max} = 0$ ,


$$R_{th} = 2R // 2R = R$$

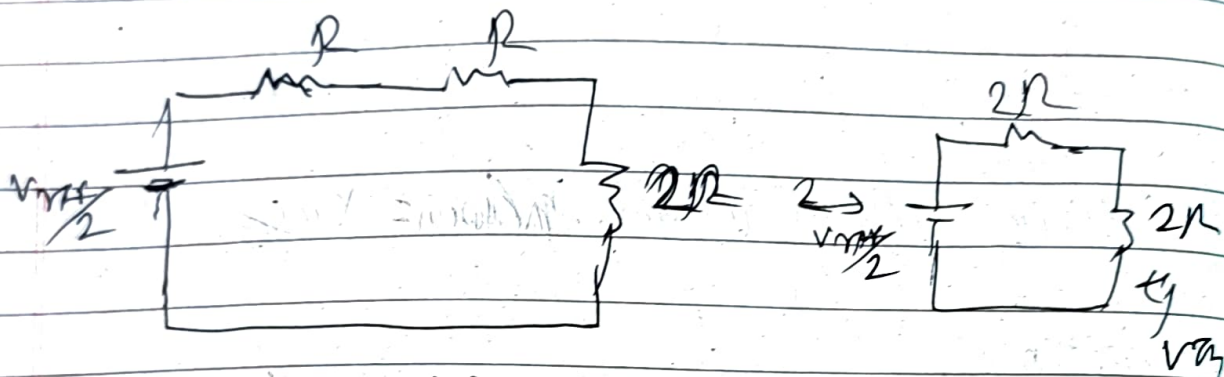

$$\therefore V_{th} = \frac{2R}{2R + 2R} \times \frac{V_{max}}{2} = \frac{V_{max}}{4}$$

Let  $V_{max}/2 = 0$

$$R_{th} = 2R // R = R$$

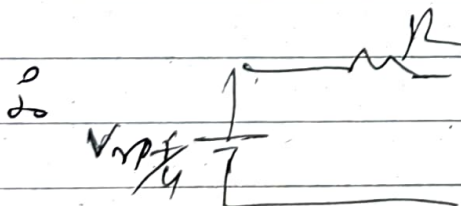

Hence, o/p of ladder network  $= \frac{V_{max}}{4}$


$$\begin{array}{lcl}
 10 & 0 & 1 \rightarrow \frac{V_{Tn}}{8} \\
 0 & 1 & 0 \rightarrow \frac{V_{Tn}}{4} \\
 1 & 0 & 0 \rightarrow \frac{V_{Tn}}{2}
 \end{array}$$

$$V_{Tn} = \frac{2R}{2R + 2R} \times \frac{V_{Tn}}{4}$$

$$V_{Tn} = \frac{V_{Tn}}{8}$$

$$\text{Let } \frac{V_{Tn}}{4} = 0$$



$$R_{in} = 2R // 2R = R$$

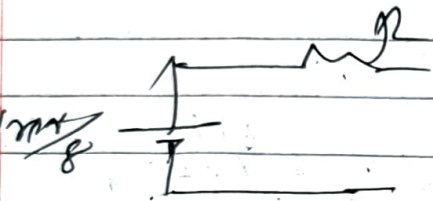



hence, o/p of ladder ~~is~~  $\frac{V_{Tn}}{8}$

Again:
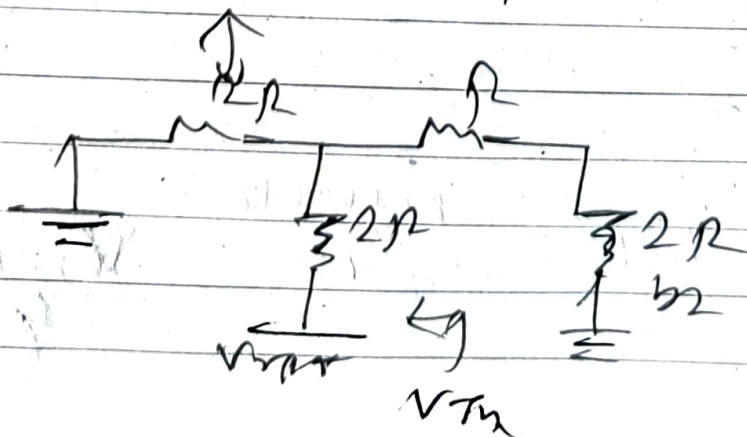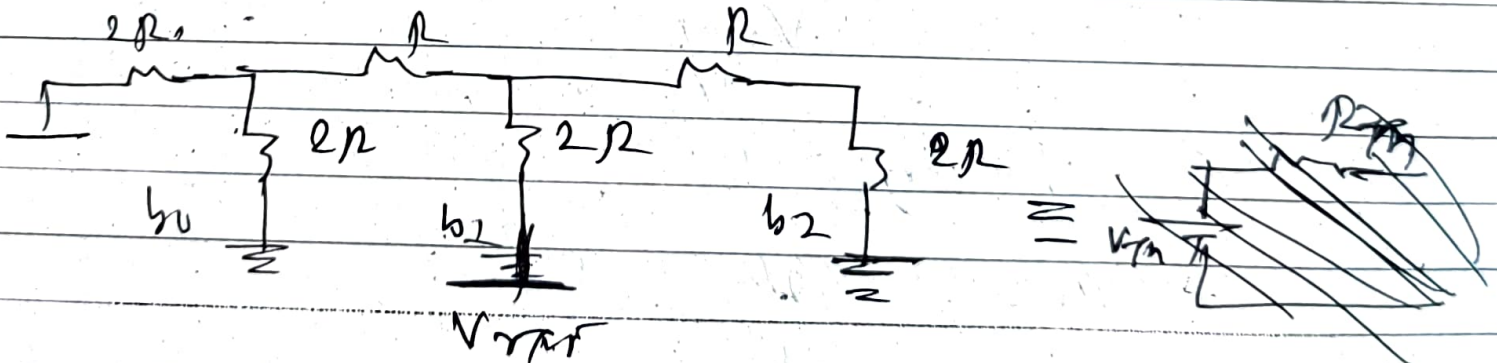
$$\begin{array}{ccc}
 b_2 & b_1 & b_0 \\
 0 & 1 & 0
 \end{array}$$





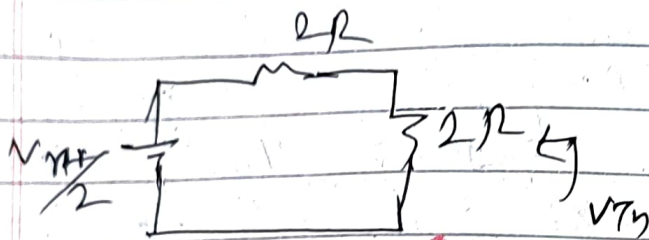
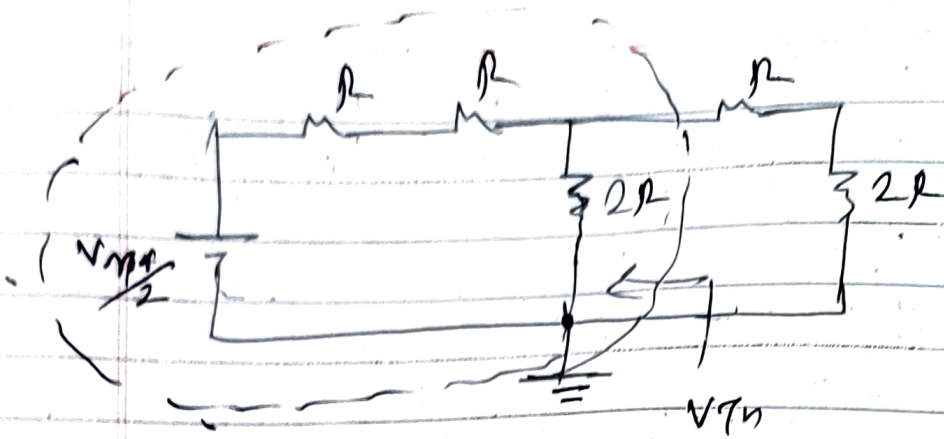


$$V_{Th} = \frac{2R}{2R + R + R} \times \frac{V_{npf}}{2}$$

$$\therefore V_{Th} = \frac{V_{npf}}{4}$$


Let  $V_{npf} = 20$

$$R_{Th} = 2R // 2R = R$$

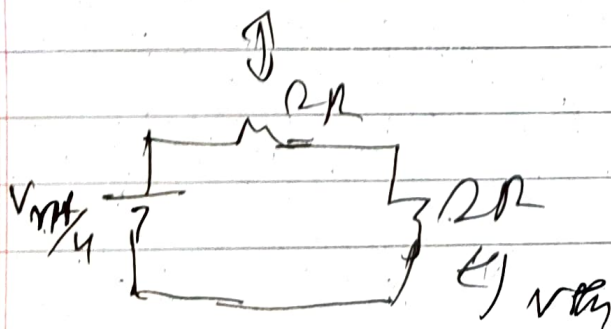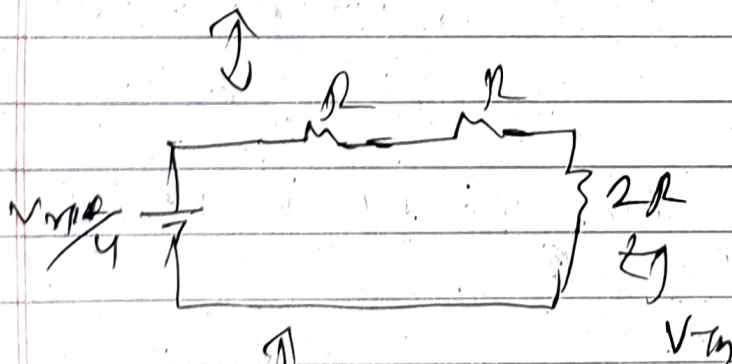

We assume at a time only one switch is on and by using superposition theorem, we find the overall o/p voltage.
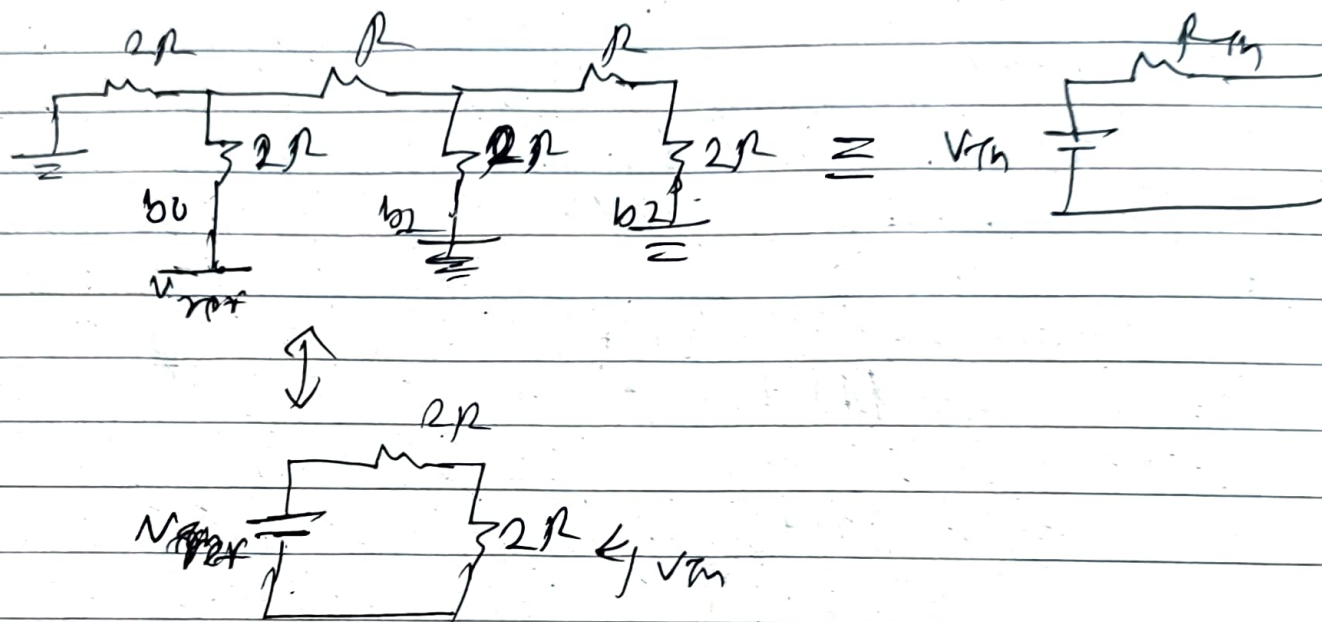
$$\begin{matrix} b_2 & b_1 & b_0 \\ 0 & 0 & 1 \end{matrix}$$



$$V_{th} = \frac{2R}{2R+2R} \times V_{ref}$$

$$V_{th} = \frac{V_{ref}}{2}$$

Let  $V_{ref} = 0$ , (To find equivalent resistance)

$$R_{th} = 2R // 2R = R$$

Vijmp

## Digital to Analogue

Date \_\_\_\_\_  
Page \_\_\_\_\_

### 2) $R-2R$ Ladder DAC (3 bits)

- uses only two values of resistors
- Easy and accurate fabrication is possible.
- Easily scalable to any desired number of bits.
- o/p resistance is  $R$ , regardless of no. of bits.


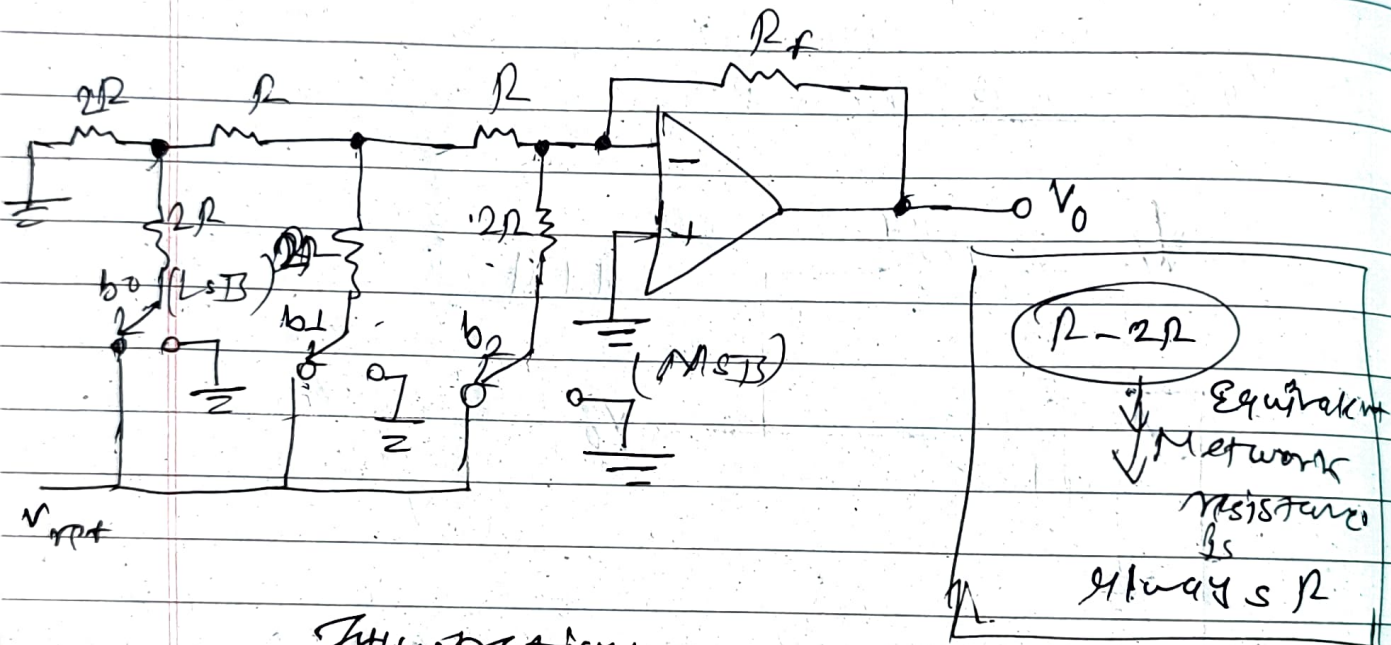


Illustration:

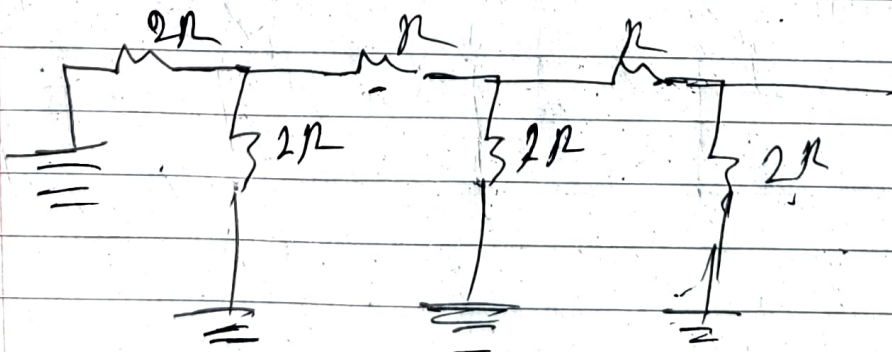$R-2R \rightarrow$  Equivalent resistance  $\rightarrow R$



$$R_{eq} = 2R_{eq} = R$$