

### Tutorial - III <Hints>

Date: / /

1) The reflected load resistance for one transistor,

$$R_L' = \left(\frac{a}{2}\right)^2 R_L \quad ; \text{ where, } a = \frac{N_1}{N_2}$$

$$N_1 = 100 ; N_2 = 50 ; R_L = 10 \Omega$$

$$a = \frac{N_1}{N_2} = \frac{100}{50} = 2$$

$$\therefore R_L' = \left(\frac{2}{2}\right)^2 \times 10 = 10 \Omega$$

For maximum output power, the collector voltage swing corresponds to  $V_{em} = V_{cc}$

The maximum output power for the two transistor is then,

$$(P_{ac})_{\text{total}} = \frac{V_{cc}^2}{2R_L'} = \frac{(20)^2}{2 \times 10} = \underline{\underline{20 \text{ watts}}}$$

max. power delivered to load.

The maximum dc power supplied to the two transistors is,

$$(P_{dc})_{\text{total}} = \frac{2V_{cc}^2}{\pi R_L'} = \frac{2 \times (20)^2}{\pi \times 10}$$

$$\therefore (P_{dc})_{\text{total}} = 25.46 \text{ W}$$

Now,

$$\text{Efficiency}(\eta) = \frac{(P_{ac})_{\text{total}}}{(P_{dc})_{\text{total}}} \times 100\%$$

$$= \frac{20}{25.46} \times 100\%$$

$$= \underline{\underline{78.55\%}}$$

2) (Same as done in class)

$$\text{o/p impedance of transistor} = \frac{\Delta V_{CE}}{\Delta I_C} = \frac{12}{100 \times 10^{-3}}$$

$$R_L' = a^2 R_L ; a = \frac{N_1}{N_2}$$

$\downarrow$   
50

$\downarrow$   
for max. power  
trf.  $= R_L'$

$$\Rightarrow a = \underline{\hspace{2cm}}$$

$$V_2 = V_L = \frac{V_1}{a} \rightarrow 12V$$

$$I_L = \frac{V_L}{R_L} = \underline{\hspace{2cm}}$$

$$\text{Power trf. to loudspeaker} = I_L^2 R_L$$

$$= \underline{\hspace{2cm}}$$

3) Done in class

4) Here,

$$R_L' = a^2 R_L ; a = \frac{N_1}{N_2} = \frac{4}{1} = 4$$

$$\therefore R_L' = (4)^2 90 = \underline{\hspace{2cm}}$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

$$\Rightarrow I_2 = I_L = I_1 \times \frac{N_1}{N_2} = I_1 \times a = \underline{\hspace{2cm}} \rightarrow 120mA$$

$$\text{Max o/p power} = I_L^2 R_L = \underline{\hspace{2cm}}$$

5) Here,

$$\text{Open loop gain } (A) = 150$$

$$\text{feedback ratio } (\beta) = 0.04$$

Open loop gain changes by 15%.

$$\text{i.e., } \frac{dA}{A} = 0.15$$

$$\frac{dA_f}{A_f} = ?$$

we know,

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{1 + \beta A} = \underline{\hspace{2cm}}$$

6) Same as Question 5)

7) Here,

$$\text{Open loop gain } (A) = 100$$

$$\text{Gain with feedback } (A_f) = 50$$

i)  $\beta = ?$ 

$$A_f = \frac{A}{1 + A\beta}$$

ii)  $\beta = \frac{\text{---}}{\text{---}}$  (maintained)

$$A_f = 75$$

$$A = 7$$

$$A_f = \frac{A}{1 + A\beta}$$

$$\Rightarrow A = \underline{\hspace{2cm}}$$



8) Here,

$$\beta = 0.2\% = 0.002$$

$$A = 60 \text{ dB}$$

$$20 \log_{10}(A) = 60 \text{ dB}$$

$$\log_{10}(A) = \frac{60}{20} = 3$$

$$\therefore A = 10^3 = 1000$$

$$\frac{dA}{A} = 15\% = 0.15$$

we know,

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{1 + \beta A}$$

$$\frac{dA_f}{A_f} = \underline{\hspace{2cm}}$$

$$9) f = 50 \text{ KHz} = 50 \times 10^3 \text{ Hz}$$

$$f = \frac{1}{2\pi RC}$$

$$\text{Let } C = 0.01 \mu\text{f}$$

then,

$$R = \underline{\hspace{2cm}}$$

Also,

$$\frac{R_f}{R_g} = 2$$

$$\text{Let } R_g = 10 \text{ k}\Omega$$

then,

$$R_f = \underline{\hspace{2cm}}$$

Draw fig.



10) Here,

$$L_1 = 3\text{mH}, L_2 = 25\mu\text{H}$$

freq. of osc. 950 kHz to 1050 kHz

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}} \quad ; \quad L_{eq} = L_1 + L_2$$

11) Here,

$$\frac{R_3}{R_4} = \frac{22\text{k}\Omega}{11\text{k}\Omega} = 2$$

$$R_3 = 2R_4$$

Since,  $R_3 = 2R_4$  (Nt:  $R_f = 2R_g$ ), the circuit will oscillate

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 5.1 \times 10^3 \times 1 \times 10^{-9}} =$$

12) Same as Question 9)

13) Here,

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}} \quad ; \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\text{feedback fraction } (\beta) = \frac{C_2}{C_1}$$