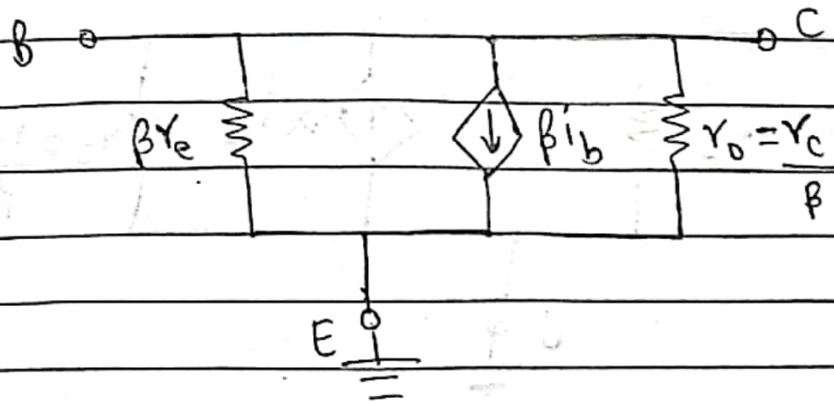



Tutorial II < Hints >

Date: / /

1) CE Bypassed




2) CE Unbypassed

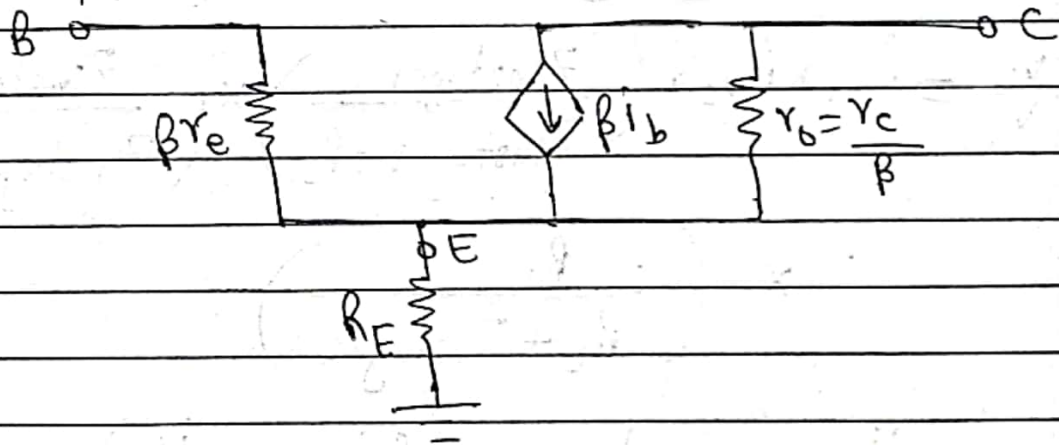


Nt:-

The value of ' r_o ' is very large and can be neglected to simplify the circuit analysis.

3) CC (common collector)

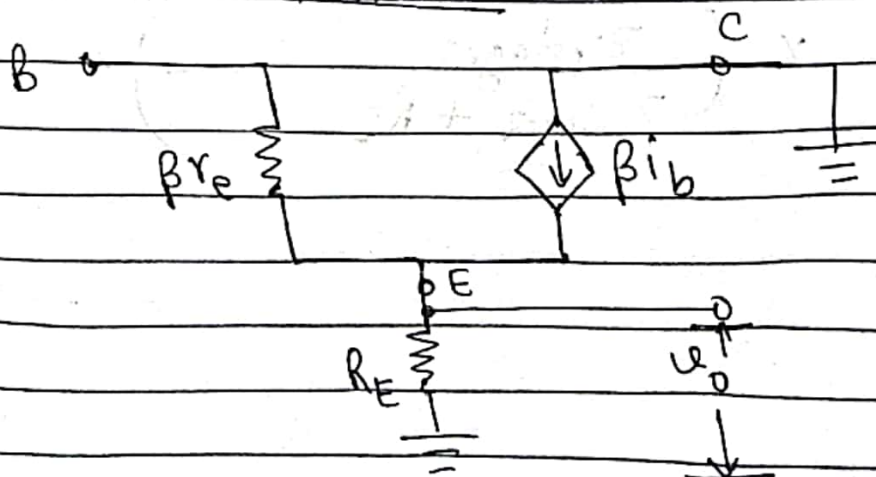

4) Common Base

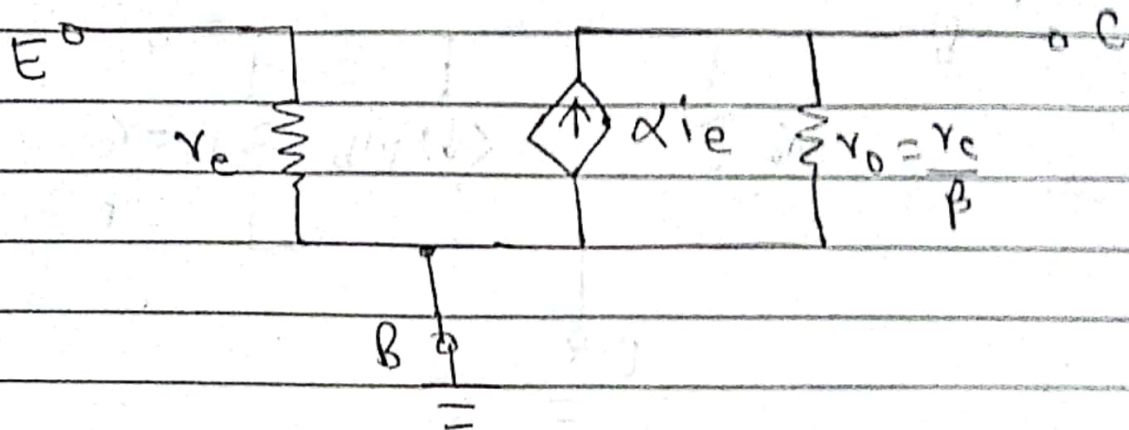

5) Overall voltage gain ($A_{vs} = \frac{V_L}{V_s}$)

$$\frac{V_L}{V_s} = A_{v1} \times A_{v2} \times \left(\frac{Z_{instage1}}{Z_{instage1} + r_s} \right) \times \left(\frac{Z_{instage2}}{Z_{instage2} + Z_{outstage1}} \right) \times \left(\frac{R_L}{R_L + Z_{outstage2}} \right)$$

6) Overall current gain ($A_{is} = \frac{i_L}{i_s}$)

$$\frac{i_L}{i_s} = A_{v1} \times A_{v2} \times \left(\frac{Z_{instage1}}{Z_{outstage1} + Z_{instage2}} \right) \times \left(\frac{Z_{instage2}}{Z_{outstage2} + R_L} \right)$$