

Chapter - 4

Operational Amplifiers

An operational amplifier is a very high gain differential amplifier with high input impedance and low output impedance. Typical uses of an op-amp are to provide voltage amplitude changes, oscillators, filter circuits and many types of instrumentation circuits. An op-amp contains a number of differential amplifier stages to achieve very high voltage gain.



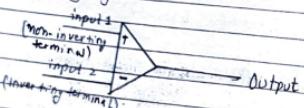


Figure shows a basic op-amp with two inputs and one output. Each input results in either the same or opposite output, depending upon whether the signal is applied to the non-inverting or inverting input respectively.

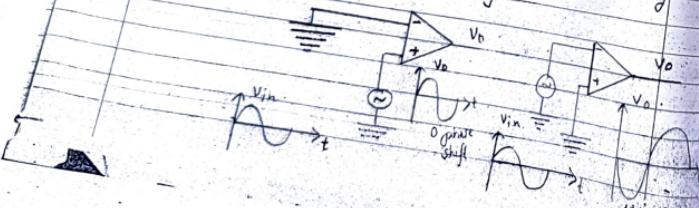

When the signal is connected to one input with the other input connected to ground (i.e. single ended input), the output will be of same polarity (in phase with input) or opposite polarity (i.e. cut-off phase) according to the input applied either to the non-inverting input or to the full inverting input respectively.

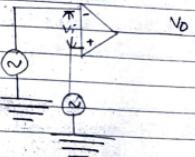When the input signal is applied to the each of the input, it is known as double-ended input.



→ multistage amplifier

Block diagram of an OP-AMP :-

An op-amp being a multistage amplifier, consists of some basic building blocks as shown in figure below :-

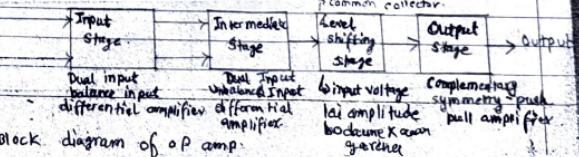


Fig : Block diagram of op amp

Characteristics of an OP-amp:

ON	Parameters	Representation	Ideal OP-amp	Practical OP-amp
1	Open loop voltage gain	A	∞	High
2	Input impedance	R_i	0	Low
3	Output impedance	R_o	0	High
4	Offset voltage (output offset)	V_{ooff}	∞	High
5	Bandwidth	$B.W$	∞	High
6	Common mode rejection ratio	CMRR	∞	High
7	Slew rate	SR	∞	High

Similarly,

- 8 It is direct coupled amplifier.
- 9 It can amplify dc and ac both type of signals.
- 10 There is virtual short circuit between the two input terminals.

Basic OP-amp circuit:-

The basic OP-amp circuit is shown in figure. An input signal V_i is applied through the resistor R_i to the following inverting input terminal.

The output voltage is feedback through resistor R_f to the same input terminal. The

non-inverting terminal is connected to the ground. Since, input voltage is applied to the inverting terminal of an OP-amp, output voltage is opposite in phase to the input signal.


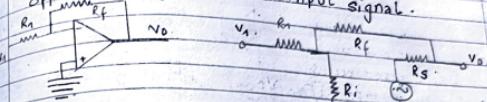


Fig: Basic OP-amp circuit

Fig: Equivalent circuit

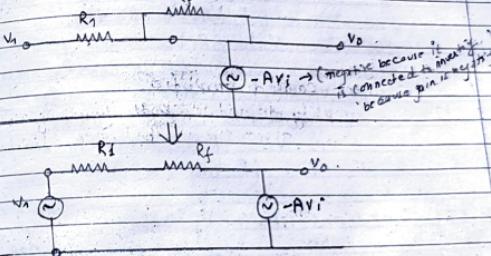
For ideal case, $R_i = \infty$ and $R_o = 0$.



For V_i , using superposition theorem,
considering source V_i only,

Here,

$$I = \frac{V_i}{R_i + R_f}$$

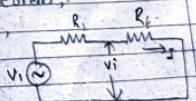

$$\therefore V_{i2} = A R_f = \frac{V_i}{R_1 + R_f} R_f \quad \text{--- (I)}$$

Again, considering source $\rightarrow V_i$ only,

$$\therefore V_{i2} = -\frac{A v_i \times R_f}{R_1 + R_f} \quad \text{--- (II)}$$

Base OP-AMP circuit :-

The total voltage,

$$v_i = V_{i1} + V_{i2}$$

$$\text{or, } V_i = \frac{V_i R_f}{R_1 + R_f} - A v_i R_1$$

$$\therefore \text{or, } V_i + A v_i \frac{V_i}{R_1 + R_f} = V_i R_f$$

$$\text{or, } V_i (R_1 + R_f) + A v_i R_1 = V_i R_f$$

$$\text{or, } V_i (R_1 + R_f + A R_1) = V_i R_f$$

$$\therefore V_i = \frac{R_f}{(R_1 + R_f + A R_1)} \cdot V_i \quad \text{--- (III)}$$

If $A \gg 1$ and $A R_1 \gg R_f$, then,

$$V_i = \frac{R_f}{A R_1} \times V_i \quad \text{--- (IV)}$$

we know, $A = -A v_o / V_i$

$$\text{or, } V_o = -A V_i = -A \times \frac{R_f}{A R_1} \times V_i$$

$$\therefore \frac{V_o}{V_i} = -\frac{R_f}{R_1} \quad \text{--- (V)}$$

Offset voltages:


i) Output offset voltage :-

The output offset voltage is the dc voltage (positive or negative) present at the output terminal when two input terminals are grounded. Ideally, the offset voltage is zero, but practically there exists a small voltage even though both the inputs are grounded.

ii) Input offset voltage :-

The voltage which is to be applied between the input terminals to make output voltage equal to zero is known as input offset voltage.

Virtual Ground:

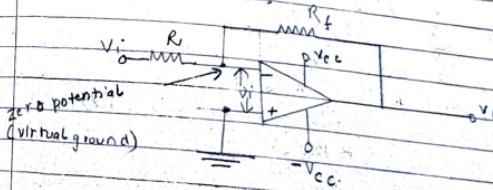

$$A = \frac{V_o}{V_i}$$

$$V_{cc} = 15V$$

$$A = \frac{V_o}{V_i}$$

$$V_i$$

$$V_i - V_{cc} = 15 = 150 \mu V$$


$$\therefore A = \frac{15}{10^5}$$

Since, $A_V = \frac{V_o}{V_i}$, the value of V_i is very small,

may be considered as 0V as compared to all other input and output. The fact $V_i = 0V$ leads to the concept that at the amplifier input there exist a virtual short circuit or virtual ground.

The concept of virtual short implies that although the voltage is nearly zero, there is no current through the amplifier input to ground.

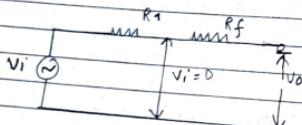
The figure below depicts the virtual ground concept. The heavy line is used to indicate that a short circuit exist with $V_i \approx 0$ but that is virtual short so no current flows through the short to ground.



The current goes only through resistor R_1 and R_f as shown in figure.

Common Mode Rejection Ratio (CMRR) :-

When the same input signal are applied to the both input, common mode operation results. A significant feature of a differential connection is that the signals that are operate opposite at inputs are highly amplified whereas those signals that are common to the two inputs are only slightly amplified. An op-amp amplify the different signal while rejecting the common signal at the two input. This operating feature is referred to as common-mode rejection.

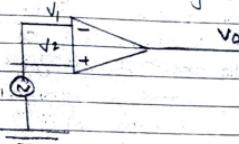

Common mode operation .

The common mode rejection ratio is defined as the ratio of differential gain to common gain.

$$\text{ie } \text{CMRR} = \frac{|A_d|}{|A_c|}$$

$$\text{In dB, } \text{CMRR}_{dB} = 20 \log \frac{|A_d|}{|A_c|}$$

Ideally, $\text{CMRR} = \infty$. This means that the common signal like noise are perfectly rejected.

jected by the amplifier.

Here, Common mode gain (A_C) = $\frac{V_o}{V_{CM}} = \frac{V_o}{\frac{V_1 + V_2}{2}}$

Differential mode gain (A_d) = $\frac{V_o}{V_1 - V_2}$.

Now, the total output of any differential amplifier can be expressed as:

$$V_o = A_d V_d + A_c V_{CN}$$

where,

$$V_d = V_1 - V_2$$

$$V_{CN} = V_1 + V_2$$

For ideal case, $A_d = \infty$ and $A_c = 0$
frequency measured

Slew Rate Measurement tells how fast output voltage changes
from small to large
is measured in $V/\mu s$

The slew rate of an op-amp is a measure of how fast the output voltage can change and is measured in Volt per microsecond ($V/\mu s$)

If the slew rate of an OP-amp is $0.5 V/\mu s$, it means that the output from the amplifier can change by $0.5 V$ every microsecond.

$$\text{Slew rate can be expressed as } SR = \frac{dV_{out}}{dt} \text{ max.}$$

Since frequency is a function of time, the slew

rate can be used to determine the maximum operating frequency of an OP-amp as:

$$f_{max} = \frac{\text{slew rate}}{2\pi \times V_p}$$

where, V_p = peak output voltage

Note

$V_o = V_p \sin \omega t$ using calculus in this eqn.

Maxⁿ rate of change,


$$|V_{oc}|(\text{max}) = V_p \omega$$

$$V_{pw} \leq SR_i$$

$$\text{or, } 2\pi f V_p \leq SR_i$$

$$f = \frac{SR_i}{2\pi \times V_p}$$

Inverting Amplifier:

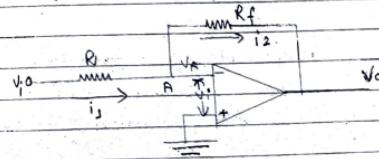

An input signal is applied through resistor R_1 to the inverting input. The output is fed back to the same inverting input through feedback resistor R_f . The non-inverting input is grounded. Since the input signal is applied to the

inverting input, the O/P will be inverted as compared to the input. Hence, the name inverting amplifier.

$$i_1 = \frac{V_i - V_o}{R}$$

$$\therefore i_1 = \frac{V_i}{R} \quad [\because V_o = 0]$$

$$i_2 = \frac{V_o - V_o}{R_f}$$

$$\therefore i_2 = -\frac{V_o}{R_f}$$


Applying KCL at node A,

$$i_1 = i_2$$

$$\text{or, } \frac{V_i}{R} = -\frac{V_o}{R_f}$$

$$\text{or, } \frac{V_o}{V_i} = -\frac{R_f}{R} \quad \therefore A_v = -\frac{R_f}{R}$$

Non-inverting Amplifier :-

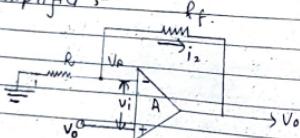

When o/p signal has to produce the same polarity as the input signal, OP-amp is connected as non-inverting amplifier as shown in figure.

$$i_1 = \frac{V_i}{R}$$

$$i_2 = \frac{V_o - V_o}{R_f}$$

we have,

$$V_i = V_1 - V_o$$

$$\text{From virtual ground, } V_i = 0$$

$$\therefore V_1 = V_o$$

$$\text{Then, } i_1 = \frac{V_1}{R}, \quad i_2 = \frac{V_1 - V_o}{R_f}$$

Applying KCL at node A,

$$i_1 + i_2 = 0$$

$$\text{or, } \frac{V_1}{R} + \frac{V_1 - V_o}{R_f} = 0$$

$$\text{or, } V_1 \left[\frac{1}{R} + \frac{1}{R_f} \right] = \frac{V_o}{R_f}$$

$$\text{or, } V_1 \left[\frac{R_f + R}{R_f R} \right] = \frac{V_o}{R_f}$$


$$\text{or, } \frac{V_1}{V_1} = \frac{R + R_f}{R_f}$$

$$\text{or, } \frac{V_o}{V_1} = 1 + \frac{R_f}{R}$$

$$\therefore A_v = 1 + \frac{R_f}{R}$$

Application of operational Amplifier:

1 OP-amp as an Adder :- i_f

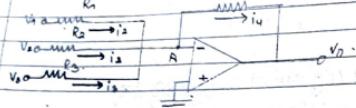

Here,

$$i_1 = \frac{V_1 - V_A}{R_1}, \quad i_2 = \frac{V_2 - V_A}{R_2}, \quad i_3 = \frac{V_3 - V_A}{R_3}, \quad i_4 = \frac{V_A - V_O}{R_f}$$

Now, Applying KCL at node A,

$$i_1 + i_2 + i_3 = i_4$$

$$\text{or, } \frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} = \frac{V_A - V_O}{R_f}$$

Since, $V_A = 0$, due to virtual ground,

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_O}{R_f}$$

$$\therefore V_O = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\text{If } R_1 = R_2 = R_3 = R_f$$

$$\therefore V_O = - \frac{R_f}{R} [V_1 + V_2 + V_3] \quad (\text{I})$$

Hence, O/P voltage is proportional to algebraic sum of three input voltages multiplied by a constant gain factor.

2 OP-amp as a subtractor:-


It provides an output proportional to one equal to the difference of two input signals.

$$\text{According to superposition theorem, } V_O = V_{O1} + V_{O2} \quad (\text{II})$$

where,

V_{O1} = O/P produced by V_1 alone.

V_{O2} = O/P produced by V_2 alone.

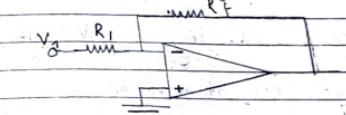


Now, considering V_1 alone,

$$V_{O1} = - \frac{R_f}{R_1} V_1 \quad (\text{III})$$

Considering V_2 alone,
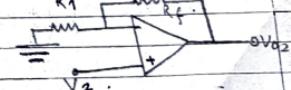
$$V_{O2} = \left(1 + \frac{R_f}{R_1} \right) V_2 \quad (\text{IV})$$



Now, From Eqn (I),

$$V_O = - \frac{R_f}{R_1} V_1 + \left(1 + \frac{R_f}{R_1} \right) V_2$$

$$= - \frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2 \quad \left[\because R_f \gg R_1, \text{ so, } \frac{R_f}{R_1} \approx 1 \right]$$

$$1 + \frac{R_f}{R_1} \approx \frac{R_f}{R_1}$$

Logic Circuit

Tutorial - 3

Boolean Algebra of Logic Gates

1) Realize all the basic gates using NAND and NOR gate.

$$\therefore V_o = \frac{R_f}{R_i} (V_2 - V_1) \quad \text{--- (IV)}$$

3) OP-amp as a differentiator :-

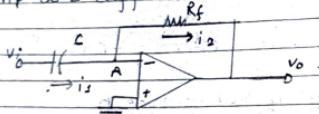


Fig : OP-amp as a differentiator

It's function is to provide O/P which is proportional to the rate of change of input voltage.

$$i_s = C \frac{d(V_i)}{dt} \quad \text{or} \quad C \frac{dV_i}{dt} = -\frac{V_o}{R_f} \quad [\because V_A = 0]$$

$$i_2 = V_A - V_o \\ R_f$$

$$\therefore V_o = -R_f C \frac{dV_i}{dt}$$

Applying KCL at node A,

$$i_s = i_2$$

$$C \frac{d(V_i)}{dt} = V_A - V_o \\ R_f$$

4) OP-amp as an integrator:-

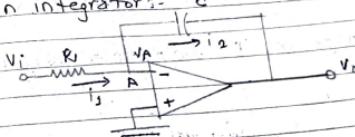


Fig : OP-amp as an integrator

It provides an output voltage proportional to the integral of input voltage.

$$i_2 = C \frac{dV_o}{dt} = -\frac{C}{R_i} V_o \quad [\because V_A = 0]$$

Applying KCL at node A,

$$i_1 = i_2$$

$$\text{or}, V_i - V_A = -\frac{C}{R_i} \frac{dV_o}{dt}$$

$$\text{or}, \frac{V_i}{R_i} = -\frac{C}{R_i} \frac{dV_o}{dt} \quad [\because V_A = 0]$$

$$\text{or}, \frac{dV_o}{dt} = -\frac{1}{RC} V_i dt$$


Integrating both sides,

$$\therefore V_o = -\frac{1}{RC} \int_0^t V_i dt$$

$$\text{Let } V_i = 10 \text{ V DC}$$

$$\therefore V_o = -\frac{1}{RC} \int_0^t 10 dt$$

(ramp signal)

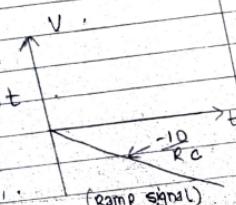

$$= -\frac{10}{R_C} t$$

Thus, note if dc voltage is applied to an integrator, it will give a ramp voltage at the output terminal.

Ramp function, $f(t) = 0$ if $t < 0$
= not if $t \geq 0$

VVI 8 or 5 marks

Instrumentation Amplifier:

Instrumentation Amplifier:

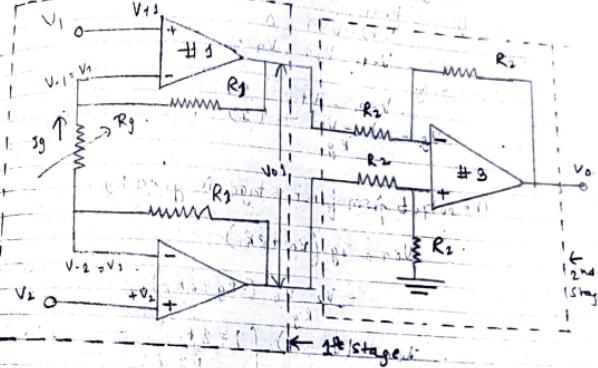


Fig: Instrumentation Amplifier.

It consists of two stages. 1st stage consists of two OP-amp. The two inputs V_1 and V_2 are applied to the non-inverting terminal of OP-amp 1 and 2 respectively and the output from 1st stage is taken through string of resistor (R_1, R_2, R_3). The two resistor R_4 and R_5 are connected internal to the IC whereas R_g is connected externally. By changing the value of R_g , the gain of I.A can be changed. So, R_g is known as gain setting resistor. Second stage is a unity gain differential amplifier.

$$V_{t+} = V_1$$

So we know,

$$V_{t+} - V_{t-} = 0$$

$$V_{t-} = V_{t+} = V_1$$

Similarly

$$V_{t-2} = V_{t+2} = V_2$$

$$I_g = \frac{V_2 - V_1}{R_g} \quad (I)$$

The output from first stage is given by :

$$V_{o1} = I_g (R_g + 2R_1)$$

$$= \frac{V_2 - V_1}{R_g} (R_g + 2R_1)$$

$$\therefore V_{o1} = \frac{(V_2 - V_1)}{R_g} (1 + 2R_1) \rightarrow II$$

As a second stage is a unity-gain differential amplifier, hence, the output is given by :

$$V_o = r V_{o1}$$

$$\text{or, } V_o = -(V_2 - V_1) \left(\frac{1 + 2R_1}{R_g} \right)$$

$$\text{or, } \frac{V_o}{V_2 - V_1} = -\left(\frac{1 + 2R_1}{R_g} \right)$$

$$\therefore A_v = \frac{V_o}{V_2 - V_1} = -\left(\frac{1 + 2R_1}{R_g} \right) \rightarrow III$$

Thus by changing the value of R_g , the

gain can be changed i.e. for higher value of R_g , the gain will be low and vice-versa.

Application of Instrumentation Amplifier:-

The IA along with the transducer bridge can be used in many applications such as :

i) Data acquisition system .

Temperature controller

Temperature Indicator .

Light Intensity System .

Data acquisition system:-

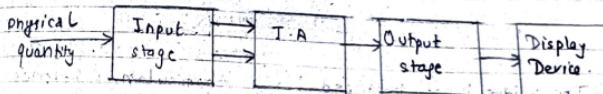


Fig : Block diagram of Data acquisition System

The transducer bridge converts physical quantity to an electrical signal. The signal is then passed to the T-A .

→ The O/P stage consists of a display device or some other conditioning circuit .

$$V+3 = V_1$$

But we know,

$$V+1 - V-1 = 0$$

$$V-1 = V+1 = V_2$$

Similarly

$$V-2 = V+2 = V_3$$

$$I_g = \frac{V_2 - V_1}{R_g} \quad (I)$$

The output from first stage is given by:

$$V_{o1} = I_g (R_g + 2R_1)$$

$$= \frac{V_2 - V_1}{R_g} (R_g + 2R_1)$$

$$\therefore V_{o1} = \left(\frac{V_2 - V_1}{R_g} \right) \left(1 + 2R_1 \right) \quad (II)$$

As a second stage is a unity-gain differential amplifier, hence, the output is given by:

$$V_o = V_{o1}$$

$$\text{Or, } V_o = -(V_2 - V_1) \left(1 + 2R_1 \right) / R_g$$

$$\text{Or, } \frac{V_o}{V_2 - V_1} = -\left(1 + 2R_1 \right) / R_g$$

$$\therefore A_v = \frac{V_o}{V_2 - V_1} = -\left(1 + 2R_1 \right) / R_g \quad (III)$$

Thus by changing the value of R_g , the

gain can be changed i.e. for higher value of R_g , the gain will be low and vice-versa.

Application of Instrumentation Amplifier:-

The IA along with the transducer bridge can be used in many applications such as:

i) Data acquisition system.

ii) Temperature controller.

iii) Temperature Indicator.

iv) Light Intensity System.


Data acquisition system:-



Fig :- Blocks diagram of Data acquisition System

The transducer bridge converts physical quantity to an electrical signal. The signal is then passed to the IA.

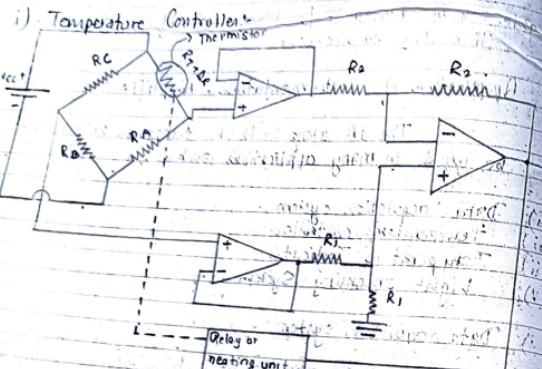The O/P stage consists of a display device or some other conditioning circuit.



- The bridge is set balanced for a particular reference temperature.
- For any change in temperature, the T.A produces the output voltage.
- This voltage can be used to drive the relay which in turn controls the ON-OFF of the heating unit to control the temperature.

ii) Temperature Indicator:

- Above figure can be used as a temperature indicator. The bridge is kept balanced at some reference temp when $V_o = 0V$.
- As the temperature changes, the amplifier output also changes.
- The meter connected at output can be calibrated to indicate the desired temperature range by selecting the appropriate gain of the amplifier.


iii) Light intensity meter:

- The circuit shown in figure above can be used as a light intensity meter if the thermister is replaced by a photocell.
- The bridge is set balanced for dark condition.
- When light falls on the photocell, its resistance changes and produces the output.
- The meter connected at the output can be calibrated in terms of LUX to measure the light intensity.

Numerical of
Instrument
based on

Numerical:

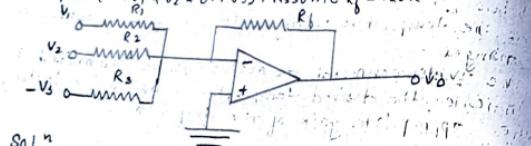Design an OP-amp adder circuit that will produce an output $(-4V_1 + V_2 - 0.1V_3)$. Assume $R_f = 100K$.



SOLⁿ

The O/P voltage of adder circuit is given by :-

$$V_0 = \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad (I)$$

Given,

$$V_0 = -(4V_1 + V_2 - 0.1V_3) \quad (\text{d. b. square})$$


Comparing eqn (I) and (II), we get

$$\frac{R_f}{R_1} = 4, \quad \frac{R_f}{R_2} = 1, \quad \frac{R_f}{R_3} = 0.1 \quad [\text{since resistor cannot be negative, } V_3 \text{ is made -ve}]$$

$$\therefore R_1 = \frac{100}{4} = 25K$$

$$R_2 = 100K$$


$$R_3 = 100/0.1 = 1000K$$

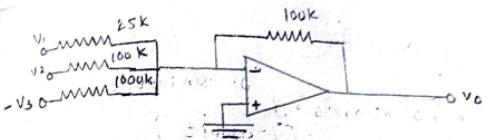


* Design an OP-amp circuit that will produce an output voltage equal to $-V_1 + 2V_2 - 3V_3 + V_u$, where V_1, V_2, V_3 & V_u are input. Assume $R_f = 100K$.

$$V_0 = -V_1 + 2V_2 - 3V_3 + V_u$$
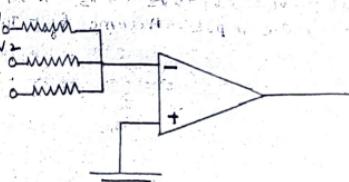
$$\therefore \frac{R_f}{R_1} = 1, \quad \frac{R_f}{R_2} = 2, \quad \frac{R_f}{R_3} = 3, \quad \frac{R_f}{R_u} = 1$$



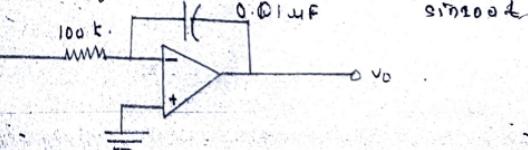* Find the peak value of the output of an ideal integrator where $R_1 = 100K$, $R_f = 100K$, $C = 0.01\mu F$ and $V_{in} = 0.5 \sin 200t$



$$v_o = -\frac{1}{Rc} \int v_{in}(t) dt$$

$$= -\frac{1}{100 \times 10^{-3} \times 0.01 \times 10^{-6}} \int 0.5 \sin 100t dt$$

$$= -\frac{0.5}{10^5 \times 0.01 \times 10^{-6}} \left[-\frac{\cos 100t}{100} \right]$$

$$= 5 \cos 100t$$

Peak value = 5V

- Q) Design an OP-amp circuit that will produce an output voltage equal to $v_o = 2v_1 + 6v_2 + 4v_3 - 12v_4$, where v_1, v_2, v_3 & v_4 are input. Assume $R_f = 100K$.